

EE3253: ELECTRICAL AND ELECTRONIC
MEASUREMENTS
LABORATORY 02

NAME : RAJAPAKSHA R.M.C.V
REG No. : EG/ 2021/ 4733
SEMESTER: 03
DATE : 20/01/2024

Table 1.1: Summative Laboratory Form

Semester	03
Module Code	EE3253
Module Name	Electrical and Electronic measurements
Lab Number	02
Lab Name	Oscilloscope Probe Testing
Lab conduction date	2023.12.0
Report Submission date	2024.01.20

Contents

1	Observation	6
1.1	Tuning the probe	6
1.1.1	Probe at x1	6
1.1.2	Probe at x10	6
1.2	Observe the output of the low impedance sine wave source.	1
1.2.1	Probe at x1	1
1.2.2	Probe at x10	3
1.3	Observe the output of high Impedance Sine wave source	6
1.3.1	Probe at x1	6
1.3.2	Probe at x10	8
1.4	Rise time & fall time of the CRO	11
1.4.1	Probe at x1	11
1.4.2	Probe at x10	11
1.5	Effect of source impedance on the rise time and fall time of the CRO	12
1.5.1	Probe at x1	12
1.5.2	Probe at x10	13
1.6	Effect of over compensation of x10 probe	14
1.7	Effect of under compensation of x10 probe	16
2	Calculation	17
2.1	Specimen Calculation	18
2.1.1	Rise time and fall time of CRO	18
2.1.2	Effect of source impedance on the rise time and fall time of CRO	19
3	Discussion	21
	Q3.What are compensation and under-compensation?	24
4	References	26

List of Tables

Table 1.1: Summative Laboratory Form	2
Table 2 : Peak to Peak Amplitudes According to Probe Positions at low impedance	1
Table 3 : Peak to Peak Amplitudes According to Probe Positions at high impedance	6

List of Figures

Figure 1 : Square wave with 1kHz and oscilloscope vertical sensitivity 5V/div	6
Figure 2 : Square wave with 1kHz and probe at 10x.....	6
Figure 3 : Output after the tuning the probe	7
Figure 4 : low impedance sine wave source Frequency at 1kHz and Probe at x1	1
Figure 5 : low impedance sine wave source Frequency at 10kHz and Probe at x1	2
Figure 6 : low impedance sine wave source Frequency at 100kHz and Probe at x1	2
Figure 7 : low impedance sine wave source frequency at 1kHz and Probe at x1.....	3
Figure 8 : low impedance sine wave source Frequency at 1kHz and Probe at x10.....	3
Figure 9 : low impedance sine wave source Frequency at 10kHz and Probe at x10.....	4
Figure 10 : low impedance sine wave source Frequency at 100kHz and Probe at x10.....	4
Figure 11 : low impedance sine wave source Frequency at 1MHz and Probe at x10	5
Figure 12 : High Impedance Sine wave source Frequency at 1kHz and Probe at x1	6
Figure 13 : High Impedance Sine wave source Frequency at 10kHz and Probe at x1	7
Figure 14 : High Impedance Sine wave source Frequency at 100kHz and Probe at x1	7
Figure 15 : High Impedance Sine wave source Frequency at 1MHz and Probe at x1	8
Figure 16 : High Impedance Sine wave source Frequency at 1kHz and Probe at x10.....	8
Figure 17 : High Impedance Sine wave source Frequency at 10kHz and Probe at x10.....	9
Figure 18 : High Impedance Sine wave source Frequency at 100kHz and Probe at x10.....	9
Figure 19 : High Impedance Sine wave source Frequency at 1MHz and Probe at x10	10
Figure 20 : 1. Rise time & fall time of the CRO in Probe at x1	11
Figure 21 : 1. Rise time & fall time of the CRO in Probe at x10	11
Figure 22 : Effect of source impedance on the rise time and fall time of the CRO Probe at x1	12
Figure 23 : Effect of source impedance on the rise time and fall time of the CRO Probe at x10	13
Figure 24 : Effect of over compensation of x10 probe rise time	14
Figure 25 : Effect of over compensation of x10 probe height of over shoot.....	15
Figure 26 : 1.1 Effect of under compensation of x10 probe Fall time.....	16
Figure 27 : Circuit diagram of oscilloscope probe	17
Figure 28 : Equivalent Circuit of The Oscilloscope Probe.....	19
Figure 29: Over compensation	24
Figure 30: Under Compensation.....	24

1 Observation

1.1 Tuning the probe

1.1.1 Probe at x1

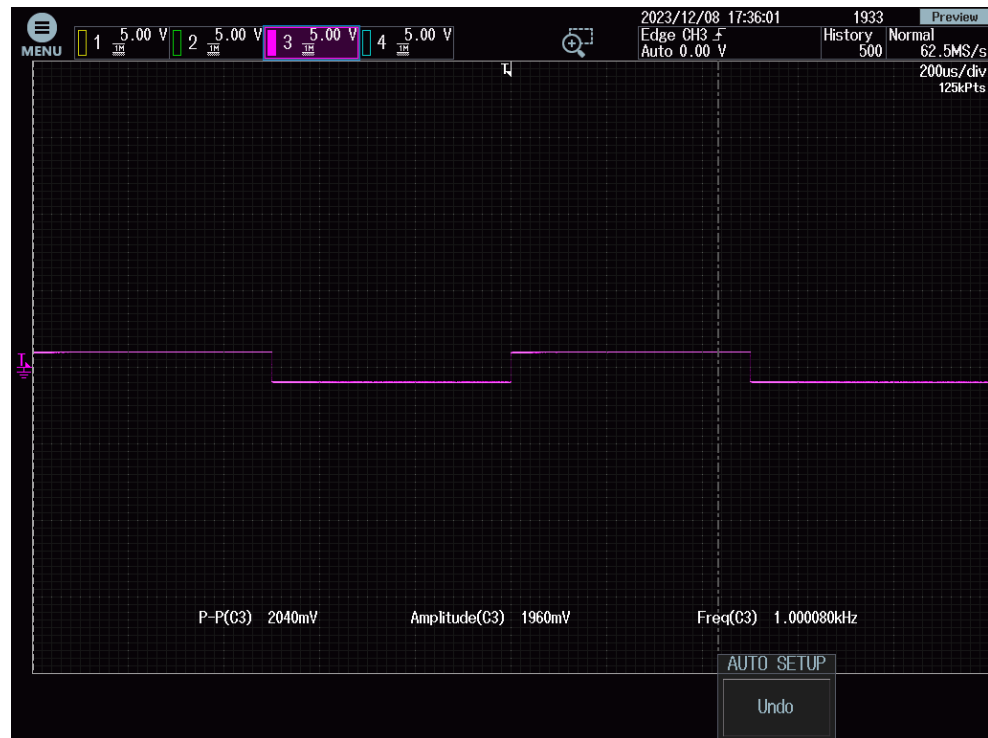


Figure 1 : Square wave with 1kHz and oscilloscope vertical sensitivity 5V/div

1.1.2 Probe at x10



Figure 2 : Square wave with 1kHz and probe at 10x

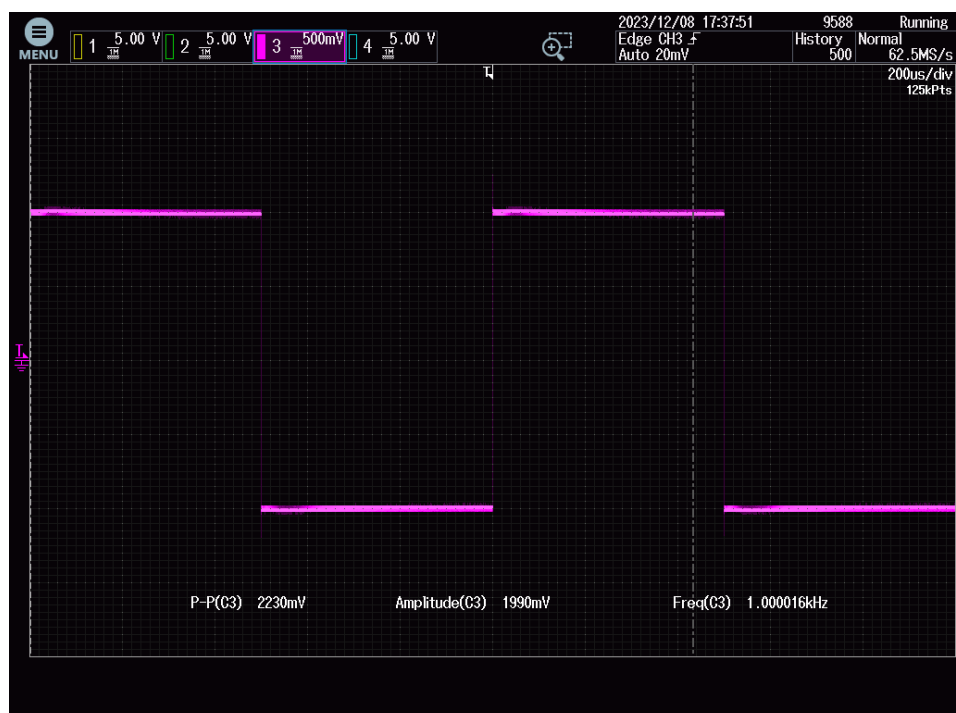


Figure 3 : Output after the tuning the probe

1.2 Observe the output of the low impedance sine wave source.

Table 2 : Peak to Peak Amplitudes According to Probe Positions at low impedance

	Probe at x1	Probe at x10
1 kHz	5.96 V	598 mV
10 kHz	5.87 V	597 mV
100 kHz	5.85 V	598 mV
1 MHz	5.93 V	610 mV

1.2.1 Probe at x1

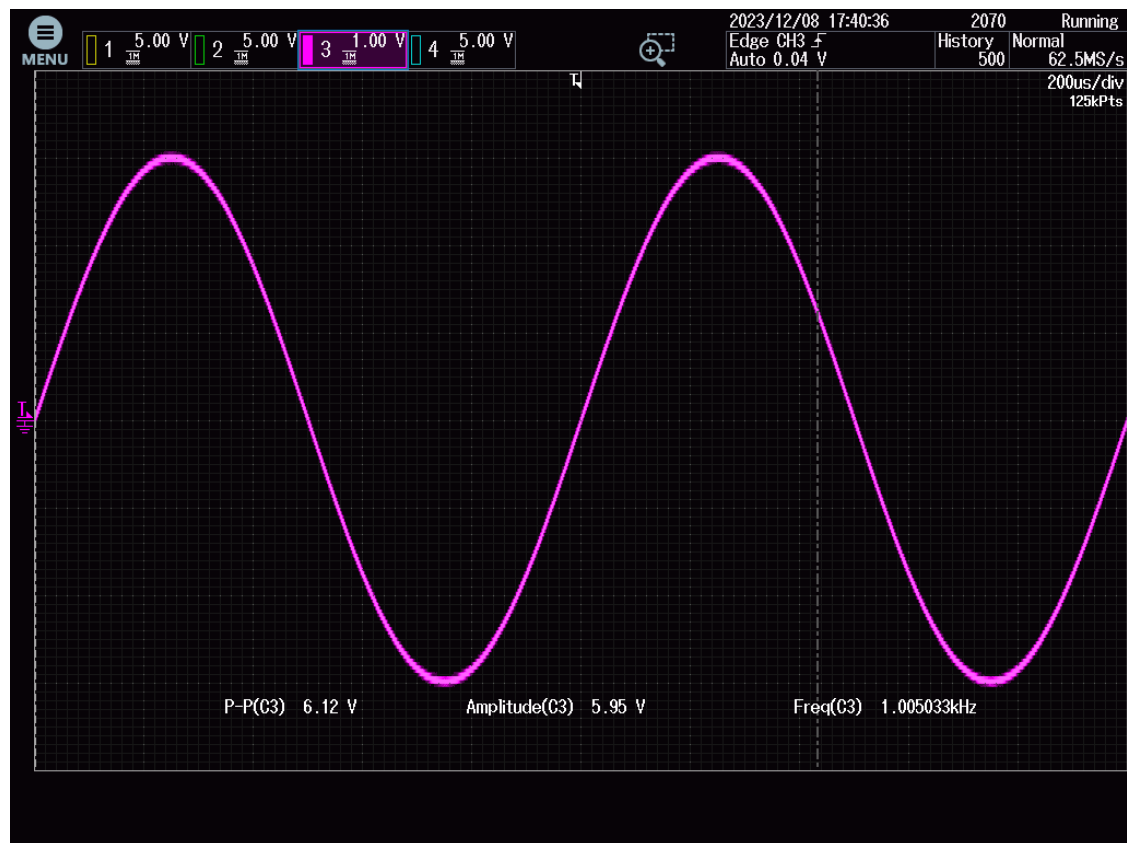


Figure 4 : low impedance sine wave source Frequency at 1kHz and Probe at x1

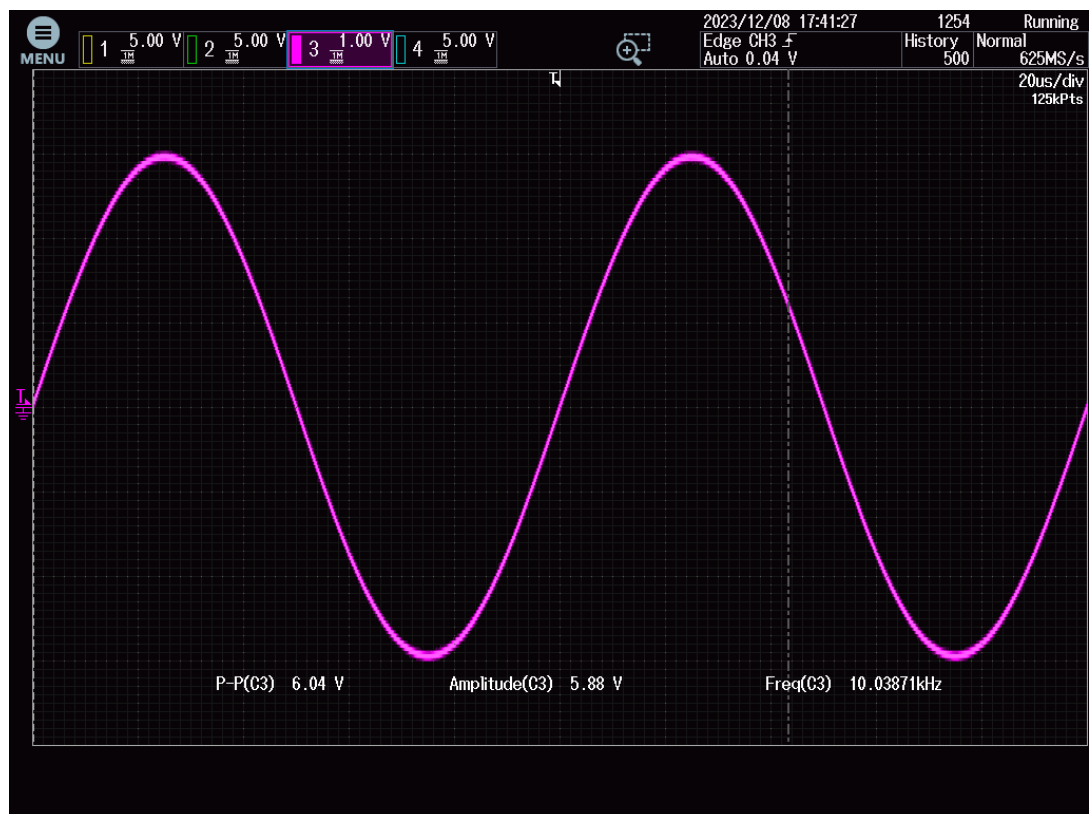


Figure 5 : low impedance sine wave source Frequency at 10kHz and Probe at x1

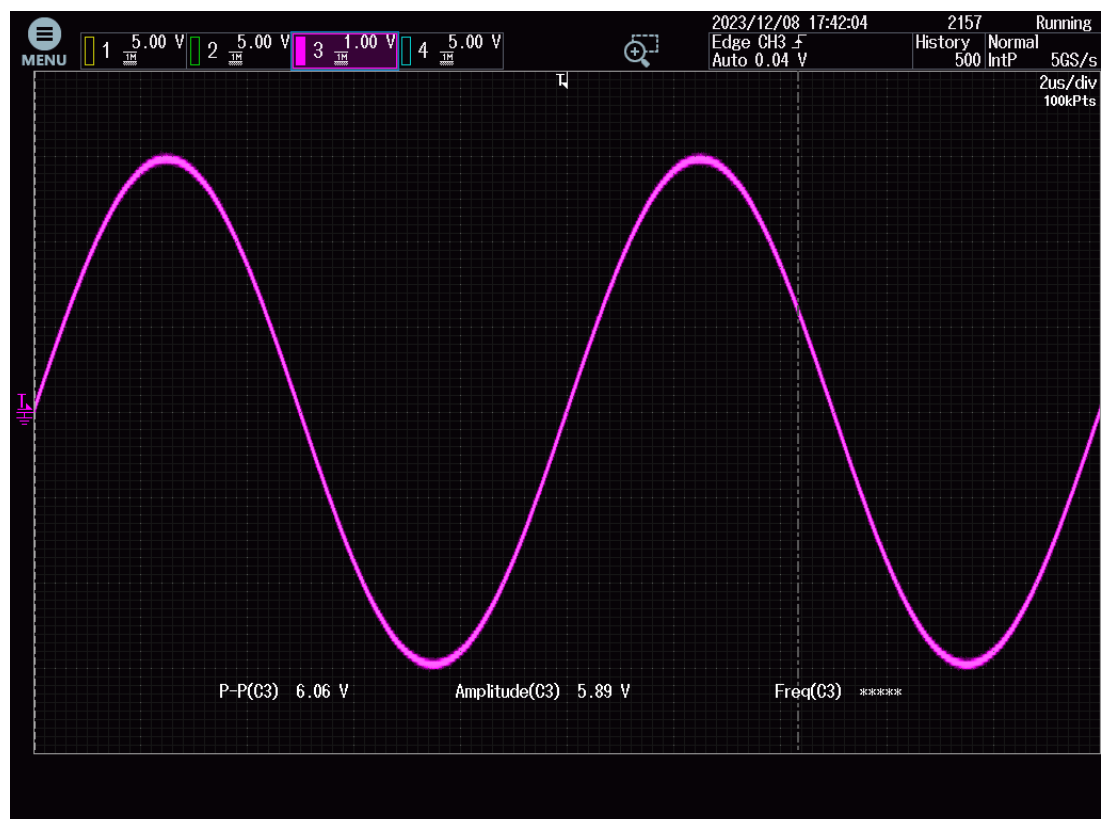


Figure 6 : low impedance sine wave source Frequency at 100kHz and Probe at x1



Figure 7 : low impedance sine wave source frequency at 1kHz and Probe at x1

1.2.2 Probe at x10



Figure 8 : low impedance sine wave source Frequency at 1kHz and Probe at x10



Figure 9 : low impedance sine wave source Frequency at 10kHz and Probe at x10



Figure 10 : low impedance sine wave source Frequency at 100kHz and Probe at x10



Figure 11 : low impedance sine wave source Frequency at 1MHz and Probe at x10

1.3 Observe the output of high Impedance Sine wave source

Table 3 : Peak to Peak Amplitudes According to Probe Positions at high impedance

	Probe at x1	Probe at x10
1 kHz	5.67 V	595 mV
10 kHz	5.34 V	594 mV
100 kHz	1720 mV	526 mV
1 MHz	185 mV	115.6 mV

1.3.1 Probe at x1

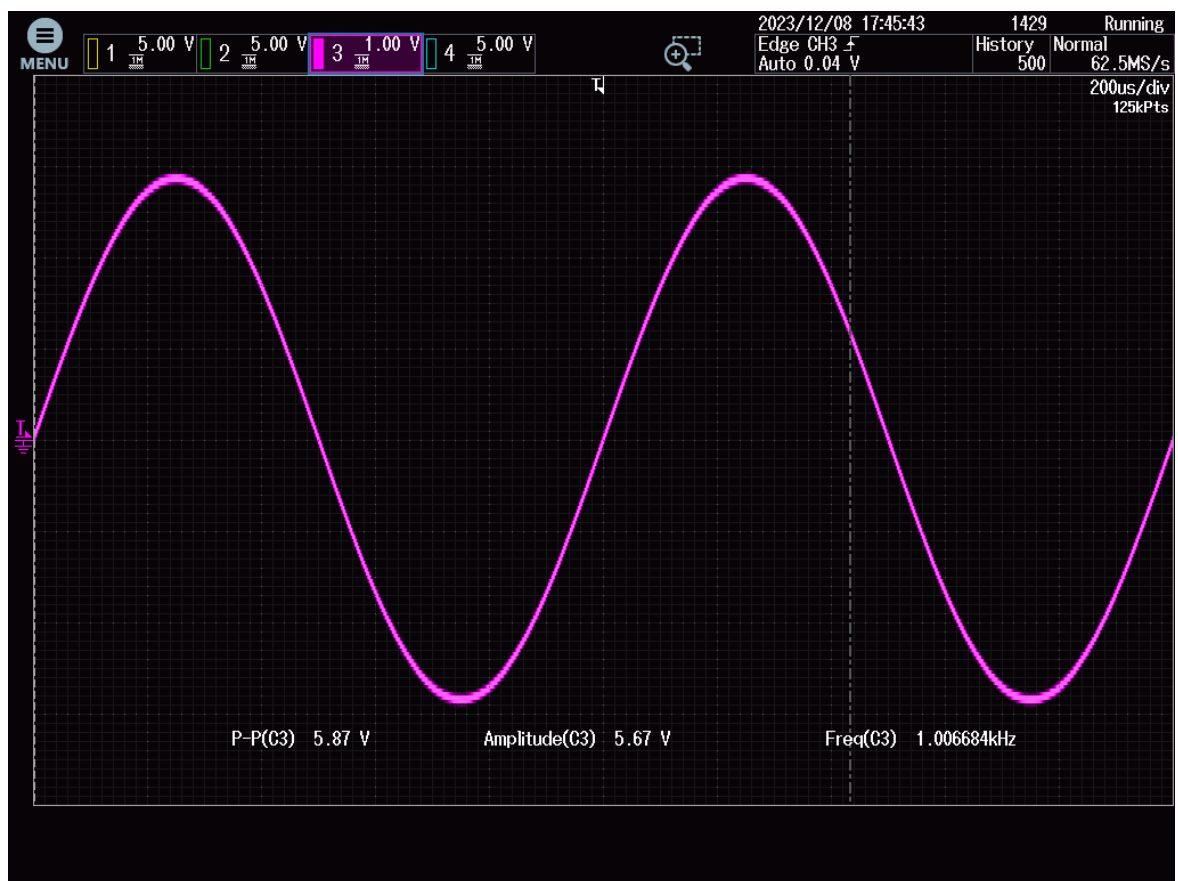


Figure 12 : High Impedance Sine wave source Frequency at 1kHz and Probe at x1



Figure 13 : High Impedance Sine wave source Frequency at 10kHz and Probe at x1



Figure 14 : High Impedance Sine wave source Frequency at 100kHz and Probe at x1

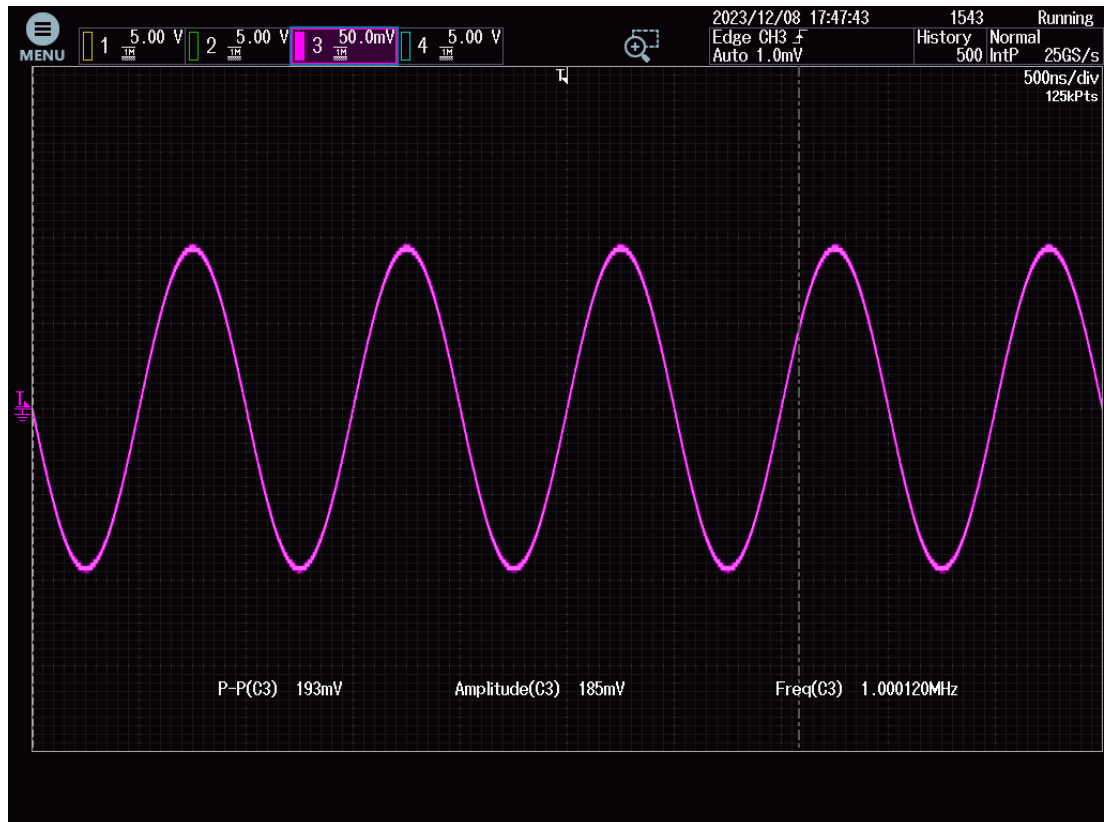


Figure 15 : High Impedance Sine wave source Frequency at 1MHz and Probe at x1

1.3.2 Probe at x10



Figure 16 : High Impedance Sine wave source Frequency at 1kHz and Probe at x10



Figure 17 : High Impedance Sine wave source Frequency at 10kHz and Probe at x10



Figure 18 : High Impedance Sine wave source Frequency at 100kHz and Probe at x10

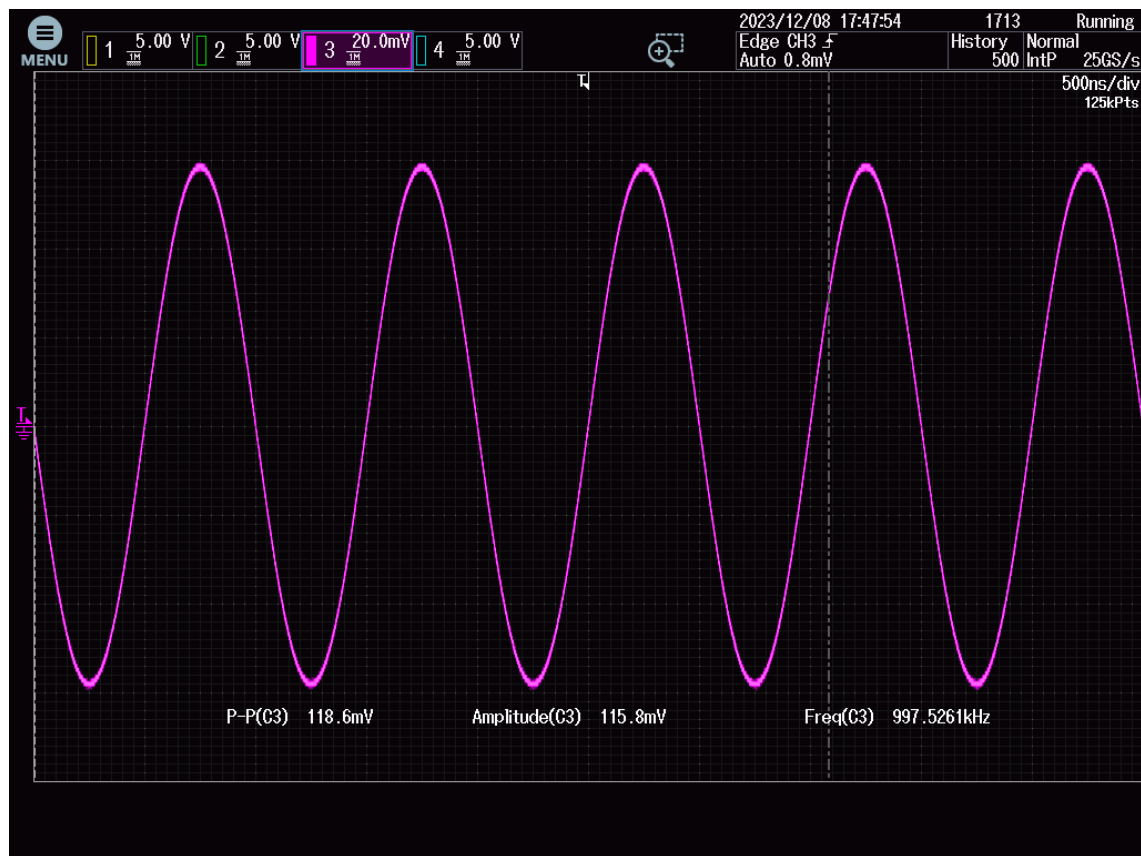


Figure 19 : High Impedance Sine wave source Frequency at 1MHz and Probe at x10

1.4 Rise time & fall time of the CRO

1.4.1 Probe at x1

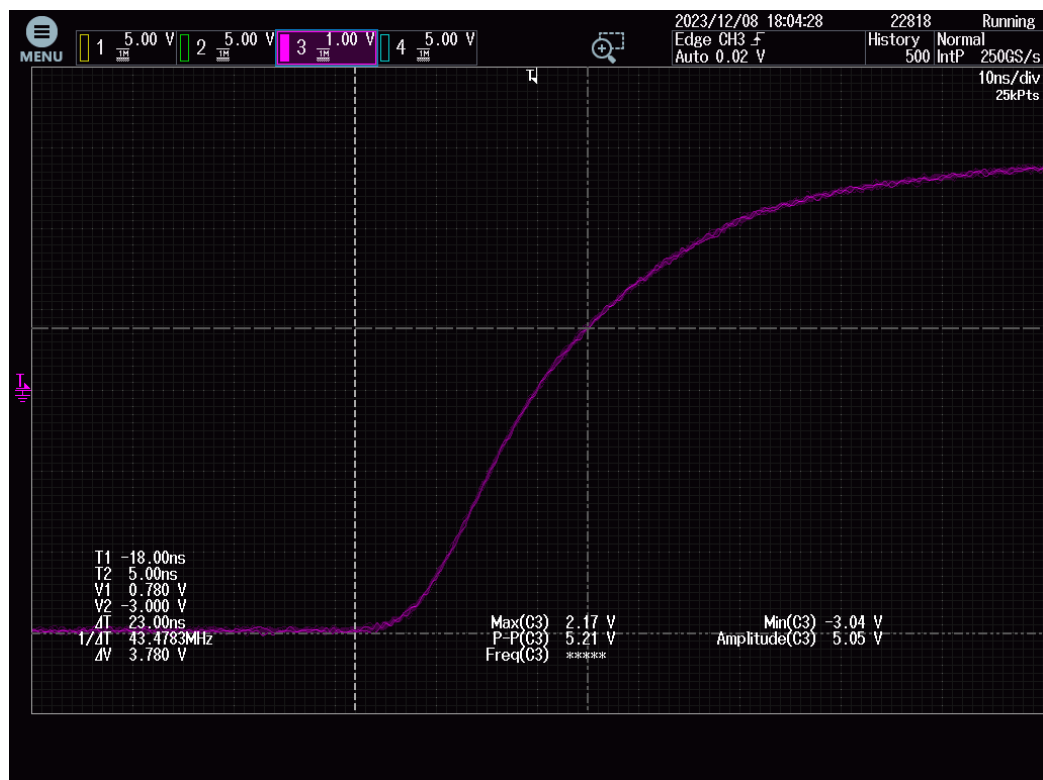


Figure 20 : 1. Rise time & fall time of the CRO in Probe at x1

1.4.2 Probe at x10

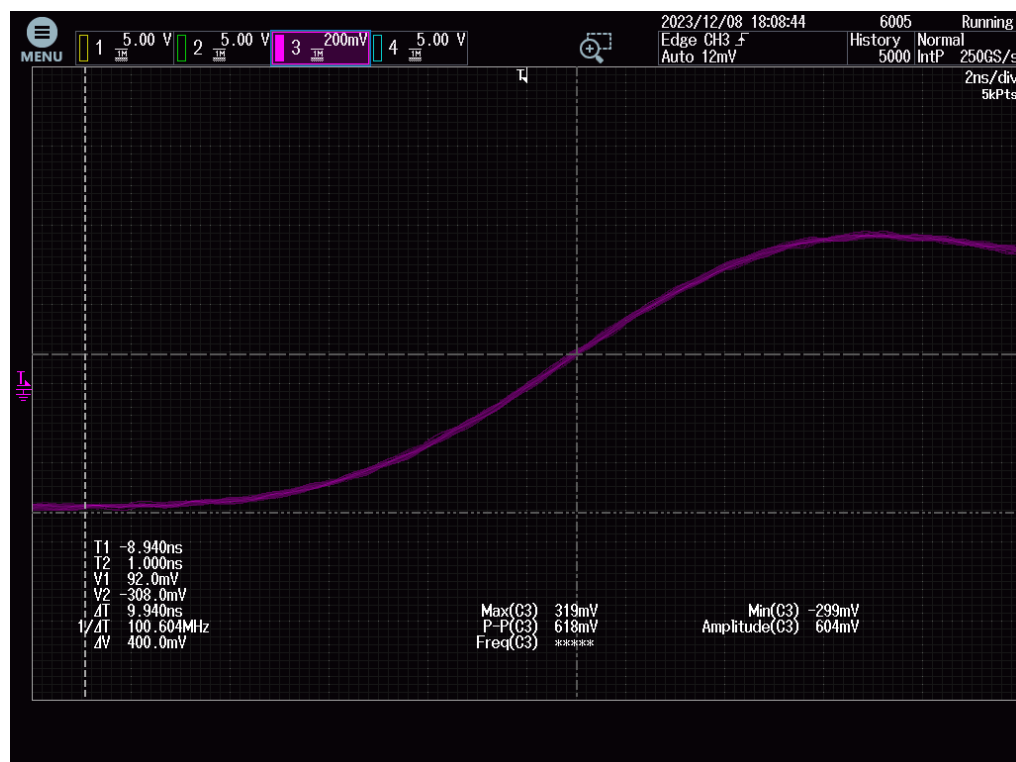


Figure 21 : 1. Rise time & fall time of the CRO in Probe at x10

1.5 Effect of source impedance on the rise time and fall time of the CRO

1.5.1 Probe at x1

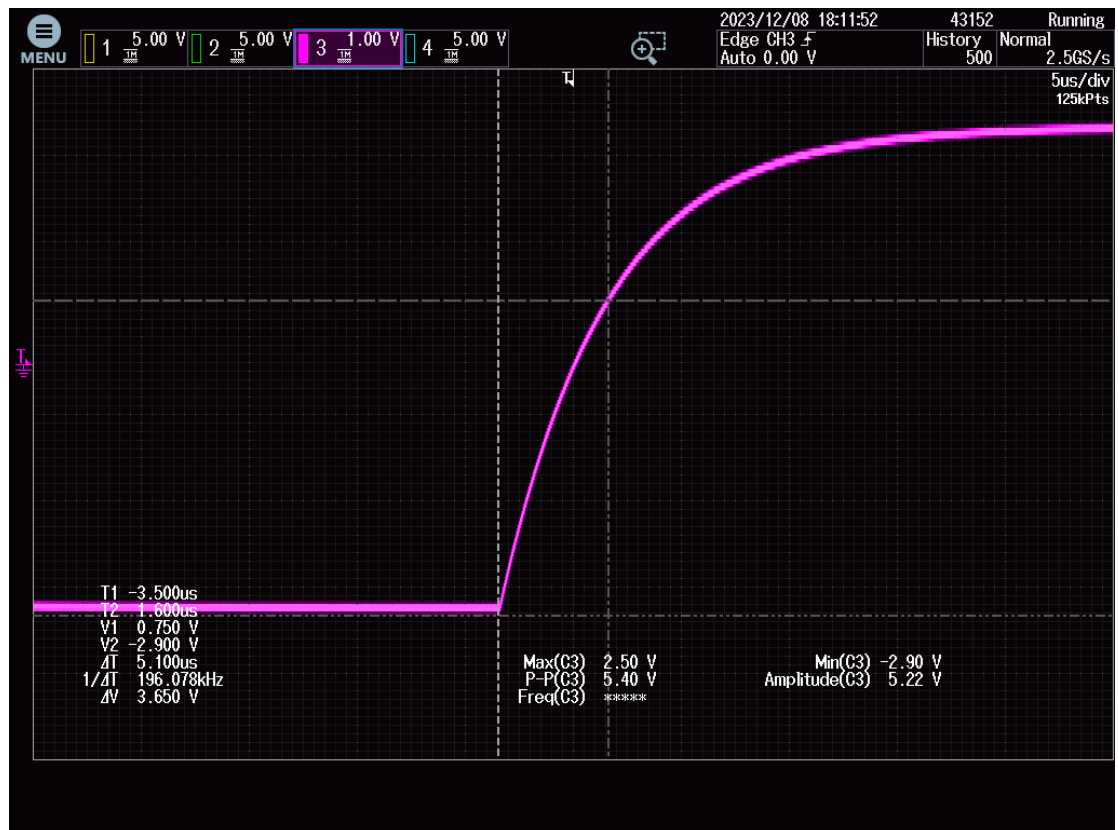


Figure 22 : Effect of source impedance on the rise time and fall time of the CRO Probe at x1

$$\begin{aligned}
 \text{Rise Time} &= T_2 - T_1 \\
 &= 1.6 \mu\text{s} - (-3.5) \mu\text{s} \\
 &= 5.100 \mu\text{s}
 \end{aligned}$$

1.5.2 Probe at x10



Figure 23 : Effect of source impedance on the rise time and fall time of the CRO Probe at x10

$$\begin{aligned}
 \text{Rise Time} &= T_2 - T_1 \\
 &= 0.260 \mu\text{s} - (-0.580) \mu\text{s} \\
 &= 0.840 \mu\text{s}
 \end{aligned}$$

1.6 Effect of over compensation of x10 probe



Figure 24 : Effect of over compensation of x10 probe rise time

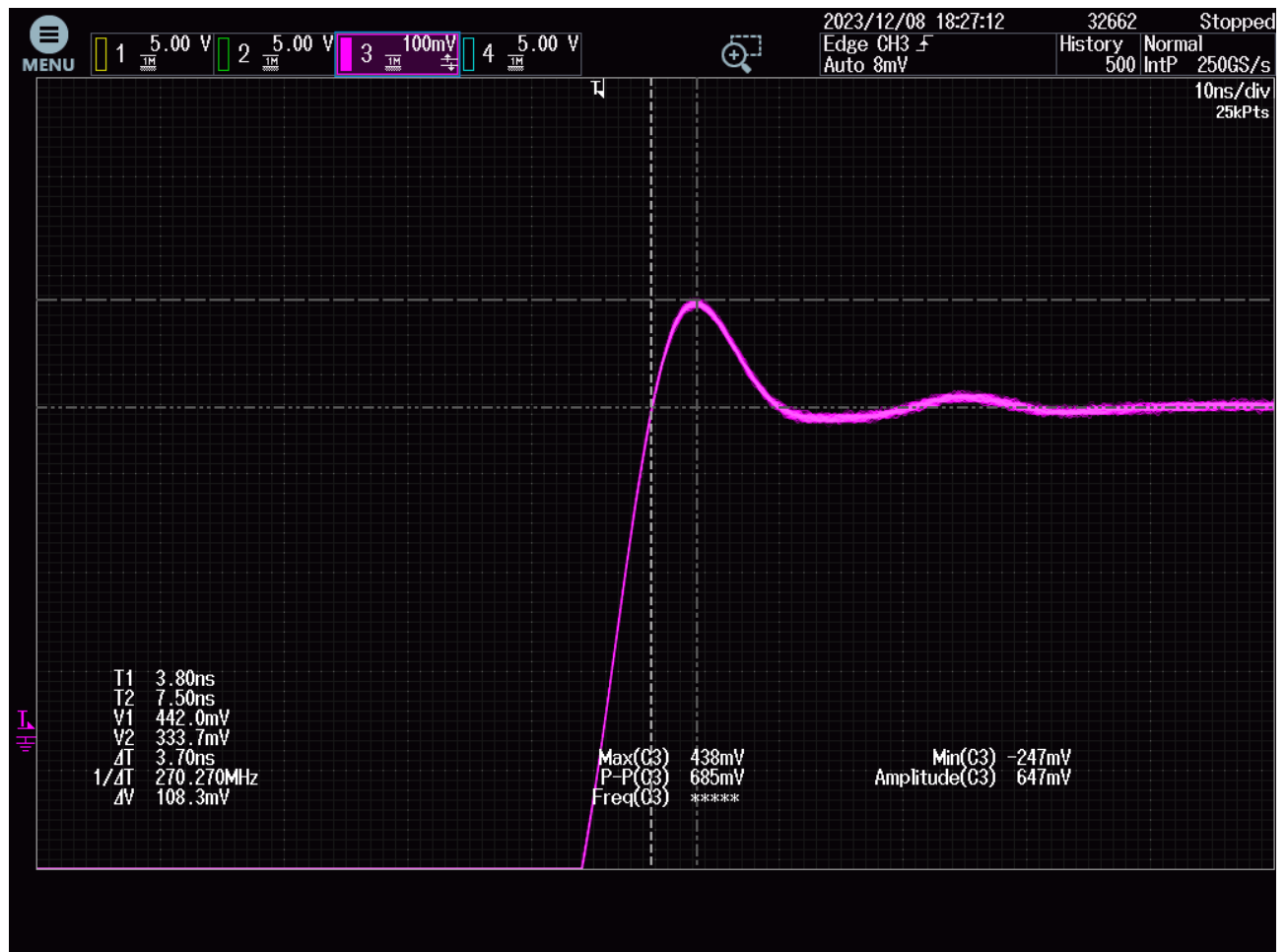


Figure 25 : Effect of over compensation of x10 probe height of over shoot

	Probe at x10
Source output voltage	$6V_{pp}$
Input voltage	685 mV
Rise time	6.60 ns
Height of over shoot	108.3 mV

1.7 Effect of under compensation of x10 probe



Figure 26 : 1.1 Effect of under compensation of x10 probe Fall time

	Probe at x10
Source output voltage	$6 V_{pp}$
Input voltage	19 mV
Fall time	10.50 ns
Height of under shoot	50 mV

2 Calculation

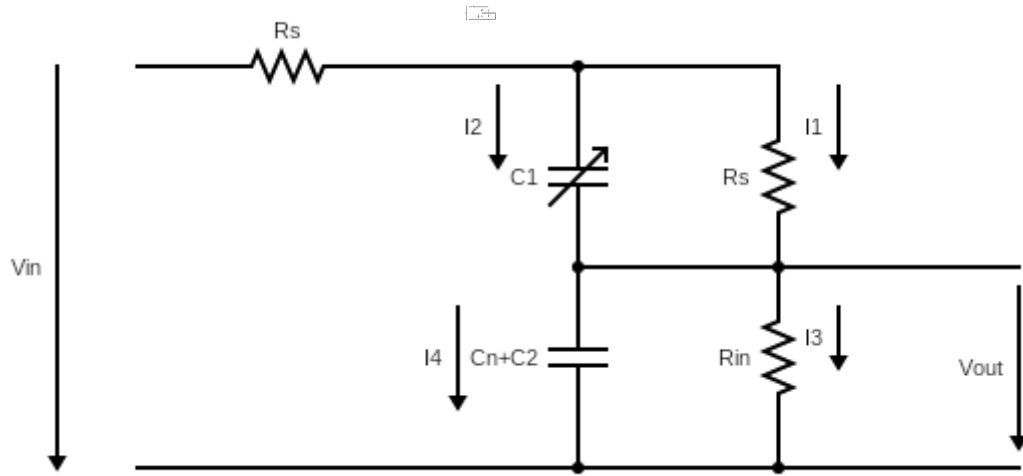


Figure 27 : Circuit diagram of oscilloscope probe

Assume the $C_2=0$

Considering above circuits

$$i_1 = C_1 \frac{dv_p}{dt}$$

$$i_2 = \frac{V_p}{R_1}$$

$$i_3 = C_2 \frac{dv_0}{dt}$$

$$i_4 = \frac{V_0}{R_2}$$

Apply the KCL low

$$I_1 + I_2 = I_3 + I_4$$

Using $I = C \frac{dV}{dt}$

Apply the KVL low

$$V_{in} = V + V_{out}$$

By using above two equations

$$\frac{V_{in}-V_{out}}{R_1} + C_1 \frac{d(V_{in}-V_{out})}{dt} = \frac{V_{out}}{R_{in}} + C_{in} \frac{dV_{out}}{dt}$$

V_{in} is constant value

$$C_1 \ll C_{in}$$

So

$$C_1 + C_{in} = C_1 = C$$

$$R_1 \lll R_{in}$$

$$\frac{1}{R_1} + \frac{1}{R_n} = \frac{1}{R_1} + \frac{1}{R}$$

We get

$$C \frac{dV_{out}}{dt} = V_{out} \times \frac{1}{R} - \frac{V_{in}}{R}$$

By solving above differential equation

$$\begin{aligned} \frac{V_{in} - V_{out}}{V_{in}} &= \frac{V_{in} - V_{in} \frac{t}{RC}}{V_{in}} \\ &= \frac{1}{1 + \frac{t}{RC}} \end{aligned}$$

$$V_{out} = V_{in} (1 - e^{-\frac{t}{RC}})$$

2.1 Specimen Calculation

2.1.1 Rise time and fall time of CRO

Considering Figure 20 for probe at \times

$$\text{Rise time} = 23.0ns$$

$$\text{Rise time} = RC$$

$$RC = 23.0ns$$

Considering Figure 21 for probe at $\times 10$

$$\text{Rise time} = RC$$

$$RC = 9.420 \text{ ns}$$

2.1.2 Effect of source impedance on the rise time and fall time of CRO

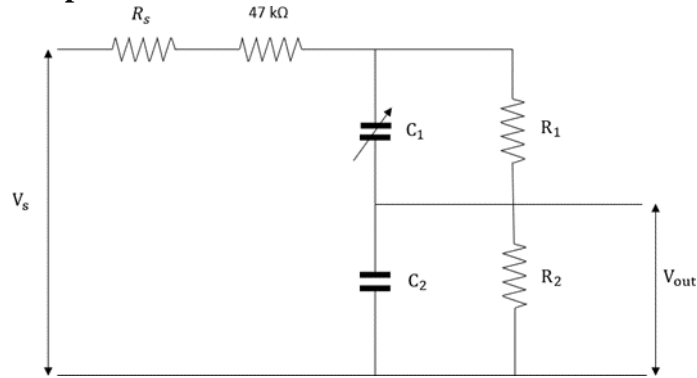


Figure 28 : Equivalent Circuit of The Oscilloscope Probe

Considering the probe at x1;

Considering Figure 22

Let's assume that the input resistance of the CRO is $1\text{M}\Omega$.;

$$V_{out} = \left[\frac{1 \times 10^6 \Omega}{R_1 + R_2 + R_s + 47 \times 10^3 \Omega} \right] V_s$$

$$5.40 \text{ V} = \left[\frac{1 \times 10^6 \Omega}{R_1 + 1 \times 10^6 \Omega + R_s + 47 \times 10^3 \Omega} \right] 6V$$

$$R_1 + R_s = 64111.111 \Omega.$$

Considering the equation;

RC = Rise time

$$RC = 5.100 \mu\text{s}$$

For the resistance R;

$$\frac{1}{R} = \frac{1}{R_2} + \frac{1}{R_1 + R_s + 47 \times 10^3 \Omega}$$

$$\frac{1}{R} = \frac{1}{10^6 \Omega} + \frac{1}{64111.11 + 47000 \Omega}$$

$$R = 1.000 \times 10^5$$

But we obtained RC as;

$$RC = 5.1 \mu\text{s}$$

Then;

$$C = (5.1 \times 10^{-6}) / 1.000 \times 10^5$$

$$C = 51.00 \text{ pF}$$

Considering the probe at x10;

Considering Figure 23

Let's assume that the input resistance of the CRO is $1\text{M}\Omega$. ;

$$V_{out} = \left[\frac{1 \times 10^6 \Omega}{R1 + R2 + Rs + 47 \times 10^3 \Omega} \right] V_s$$

$$605 \text{ mV} = \left[\frac{1 \times 10^6 \Omega}{R1 + 1 \times 10^6 \Omega + Rs + 47 \times 10^3 \Omega} \right] 6V$$

$$R1 + Rs = 8.8703 \text{ M}\Omega.$$

Considering the equation;

RC = Rise time

$$RC = 0.840 \mu s$$

For the resistance R;

$$\frac{1}{R.} = \frac{1}{R2.} + \frac{1}{R1 + Rs + 47 \times 10^3 \Omega.}$$

$$\frac{1}{R} = \frac{1}{10^6} + \frac{1}{8.8703 \text{ M}\Omega + 47000 \Omega}$$

$$R = 900.90 \text{ k}\Omega$$

But we obtained RC as;

$$RC = 5003.955 \text{ ns}$$

Then;

$$C = (0.840 \times 10^{-6} \text{ s}) / 900.90 \text{ k}\Omega$$

$$C = 0.932 \text{ pF}$$

3 Tabulation

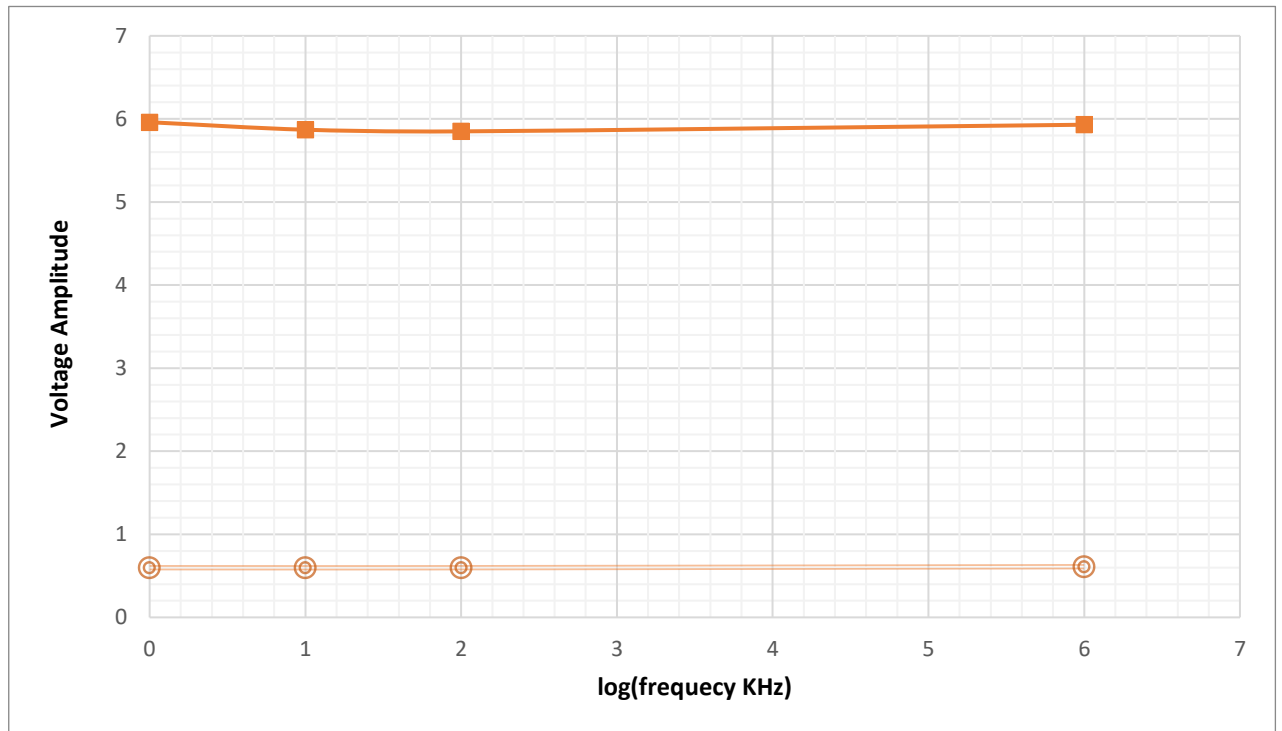


Figure 29 : The graph of amplitude vs log frequency for low impedance sine wave source

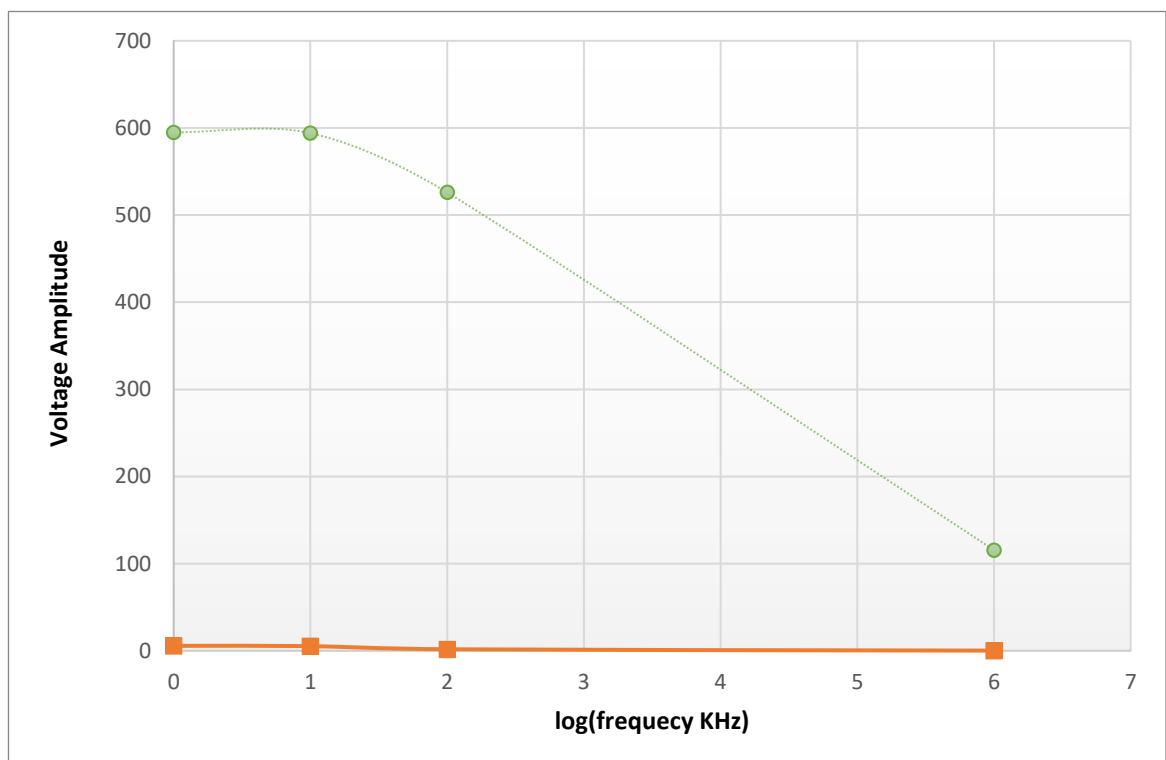


Figure 30 : The graph of amplitude vs log frequency for high impedance sine wave source

4 Discussion

Q1. What is rise time?

Rise time is defined as the time taken for a signal to cross from a specific low value to a specified high value. In practice, the specified lower value and the specified higher value are 0% and 63% of the final steady values. So rise time can be defined as how long it takes for a signal to go from 0% to 63% of its final value.

Mathematically, rise time (t_r) is defined as the time it takes for the signal to rise from the lower threshold (V_L) to the upper thresholds (V_H), and it is measured between the points where the signal crosses these thresholds.

$$t_r = t_H + t_L$$

The rise time is a critical parameter in analog and digital systems. It describes the time taken for the output to rise from one level to another in another system, which has many real-world implications. The rise time represents how long a signal spends in the intermediate state between two reference logic levels. In a digital system. [1]

Q2. Discuss the effect of source impedance on the rise time and fall time.

The electrical resistance or reactance of the source generating the signal is known as the source impedance. It may have an impact on a signal's rise time and fall time, which indicate how quickly a signal changes levels.

The source impedance is the electrical resistance or reactance of the source that is producing the signal. It might affect a signal's rise time and fall time, which show how fast a signal shifts in strength.

Take into consideration, for instance, a circuit powered by a signal source with a high source impedance and a load capacitance. The load capacitance can only be charged or discharged with a limited amount of current due to the high source impedance. This will cause the signal's rise and fall times to be slower. The signal will rise and fall more quickly, however, if the signal source has a low source impedance because more current will be available to charge or discharge the load capacitance.

The load impedance of the circuit, the rise and fall times of the signal source, and the bandwidth of the circuit can all have an impact on a signal's rise and fall times in addition to the source impedance. Engineers need to take these things into account when planning and maximizing systems customized for particular uses.

Q3.What are compensation and under-compensation?

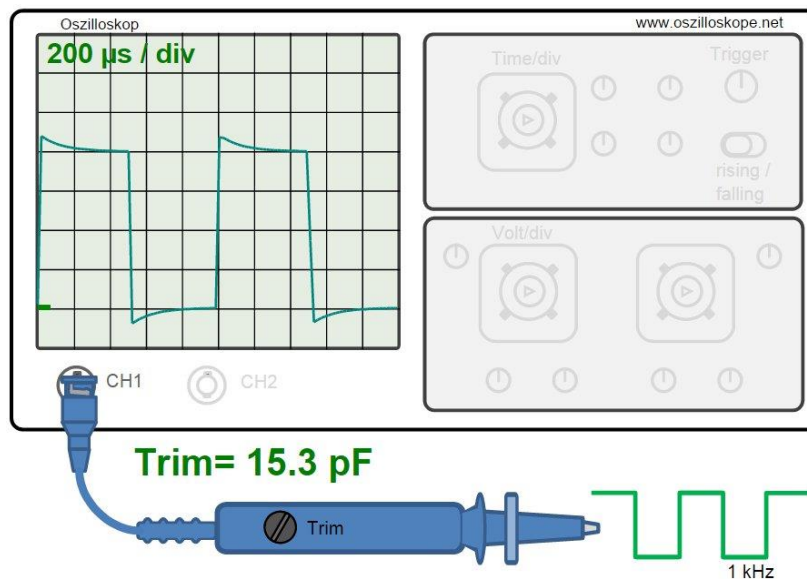


Figure 31: Over compensation

In Figure 31 you can see the over-compensation wave. Overcompensation occurs when the trim capacity is too high. In this case, the rising edge shoots above the target value. The falling edge goes below the zero level before the curve slowly approaches the zero line. We can use the observations.

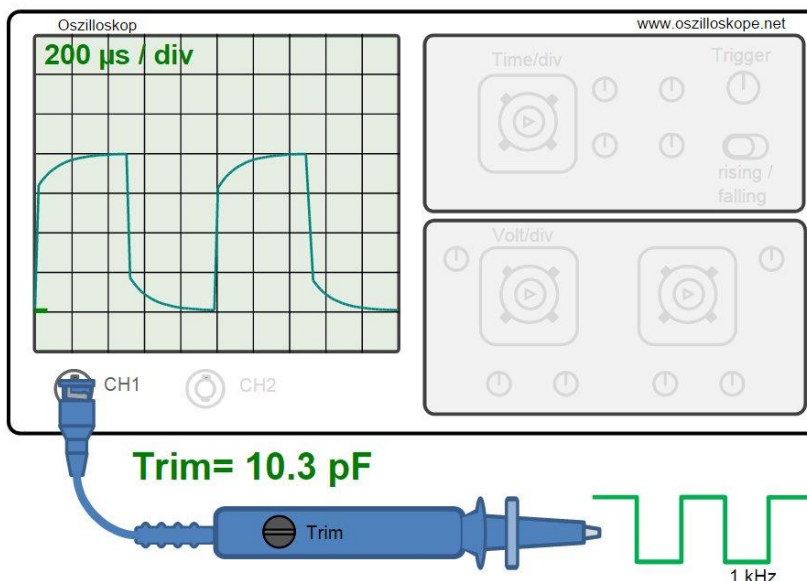


Figure 32: Under Compensation

The figure simulates the observed input signal at the oscilloscope in the case of a square wave voltage present at a frequency of 1000 Hz. The scenario of inadequate compensation is depicted in the simulation. The capacitor's cutting capacitance is inadequate. The signal is rising and declining too slowly. [2]

Q4. What are the reason/reasons for over-compensation and under-compensation?

There are many reasons for over and under-compensation. Some of them are

- Frequency Response Issues
- Ringing
- Attenuation of High Frequencies
- Roll-Off

Overcompensation happens when the compensation is set very high. This may result in a probe that is too fast for the actual system being measured. Because of that, high-frequency components of the signal may be distorted or attenuated. Overcompensation can cause the signal to overshoot and undershoot, ringing the waveform. Because of this, precisely analysing the waveform may be difficult.

The probe might not be able to adequately adjust for the high-frequency components of the signal if the compensation is set too low. At higher frequencies, this may lead to a loss of signal fidelity. Inaccurate amplitude measurements for high-frequency components can result from under-compensation, which can produce a roll-off in the frequency response.

5 References

- [1] Sweetwater, "Rise Time/Fall Time,," inSync, 2006. [Online]. Available:
] <https://www.sweetwater.com/insync/rise-time-fall-time/#:~:text=Rise%20time%20is%20typically%20measured,value%20to%20the%20lowest%20value..> [Accessed 11 January 2024].
- [2] Oszi-Admin, "Probe compensation,," Oszilloskope.net., 2019. [Online]. Available:
<https://www.oszilloskope.net/en/probe-compensation/>. [Accessed 05 January 2014].

